

00 Efficiency of Rectifier and Efficiency of half  
 01 wave and full wave rectifier:

10 Efficiency of rectifier is defined as the ratio  
 11 of DC power to the applied input AC power

$$\text{Rectifier Efficiency} = \frac{\text{DC output power}}{\text{AC input power}}$$

$$\Rightarrow \eta = \frac{P_{dc}}{P_{ac}}$$

02  
 03  
 04 \*Efficiency of Half wave rectifier:

05 In half wave rectifier,

$$P_{dc} = I_{dc}^2 R_L \quad \text{--- (1)}$$

06 Where  $R_L$  is load resistance  
 of half wave rectifier  
 circuit

07 But  $I_{dc} = \frac{I_0}{\pi}$  where  $I_0$  is peak value of AC

using (2) in (1)

$$P_{dc} = \left(\frac{I_0}{\pi}\right)^2 R_L$$

$$\Rightarrow P_{dc} = \frac{I_0^2}{\pi^2} R_L \quad \text{--- (11)}$$

$$\text{Now } P_{ac} = I_{rms}^2 (R_L + r_d)$$

where  $r_d$  is diode resistance.

When  $R_L \gg r_d$ , then  $R_L + r_d \approx R_L$

$$\text{So, } P_{ac} = I_{rms}^2 R_L \quad \text{--- (iv)}$$

$$\text{Now } I_{rms} = \frac{I_0}{2} \quad \text{--- (v)}$$

using (v) in (iv)

$$P_{ac} = \left(\frac{I_0}{2}\right)^2 R_L$$

$$\Rightarrow P_{ac} = \frac{I_0^2}{4} R_L \quad \text{--- (vi)}$$

$$\text{As } \eta = \frac{P_{dc}}{P_{ac}} \quad \text{--- (vii)}$$

using (vi) and (v) in (vii), we get

$$\eta = \frac{\frac{I_0^2 R_L}{4}}{\frac{I_0^2 R_L}{4}}$$

$$\Rightarrow \eta = \frac{4}{12} = 0.406 = 40.6\%$$

### ⊙ Efficiency of Fullwave Rectifier:—

AS  $P_{dc} = I_{dc}^2 R_L$  (i) [When  $R_L$  is the load resistance of fullwave rectifier etc.]

For full wave rectifier,

$$I_{dc} = \frac{2I_0}{\pi} \quad \text{--- (ii)}$$

Using (ii) in (i) we get

$$P_{dc} = \left(\frac{2I_0}{\pi}\right)^2 R_L$$

$$\Rightarrow P_{dc} = \frac{4I_0^2}{\pi^2} R_L \quad \text{--- (iii)}$$

Now  $P_{ac} = I_{rms}^2 (R_L + r_d)$  [ $r_d \Rightarrow$  Diode resistance]

AS  $R_L \gg r_d$  so  $R_L + r_d \approx R_L$

$$\Rightarrow P_{ac} = I_{rms}^2 R_L \quad \text{--- (iv)}$$

For full wave rectifier,

$$I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{--- (v)}$$

Using (v) in (iv)

$$P_{ac} = \left(\frac{I_0}{\sqrt{2}}\right)^2 R_L$$

$$\Rightarrow P_{ac} = \frac{I_0^2}{2} R_L \quad \text{--- (vi)}$$

January


MONDAY

5th Week - 027-339

$$A3 \eta = \frac{P_{dc}}{P_{ac}} = \frac{4I_o^2 R_L}{\pi^2 I_o^2 R_L} = \frac{8}{\pi^2}$$

$$\eta = 0.812 = 81.2\%$$

## Capacitor Filter (C-filter)

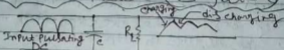

A capacitor-input filter is a filter ckt in which the first element is capacitor connected in parallel with the output of the rectifier in a linear power supply. The capacitor increases the dc voltage and decreases the ripple voltage components of the output. The capacitor is often referred to as a smoothing capacitor. The capacitor is often followed by other alternating series and parallel alternating filter elements to further reduce ripple voltage, or adjust dc voltage. It may also be followed by a voltage regulator which virtually eliminates any remaining ripple voltage and adjusts the dc voltage output very precisely to match the dc voltage required by the ckt.

2020 FEBRUARY

Mo T W T F S S

1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30	31				

01 Operation: - During the time the rectifier is conducting  
 02 and the potential is higher than the charge across the  
 03 capacitor, the capacitor will store energy from the  
 04 transformer, when the output of the rectifier falls  
 05 below the charge on the capacitor, the capacitor will  
 06 discharge energy into the ckt. Since the rectifier  
 07 conducts current only in the forward direction, any  
 08 energy discharged by the capacitor will flow into the  
 09 load. This results in output of a DC voltage upon  
 10 which is superimposed a waveform referred to as a  
 11 sawtooth wave is a convenient linear approximation  
 12 to the actual waveform which is exponential  
 13 for both charge and discharge. The crests  
 14 of the sawtooth wave will be more rounded  
 15 when the dc resistance of the transformer  
 16 secondary is higher. The time constant  $R_L C$  will be  
 17 large. The reactance is very very less than  
 18 ~~than  $R_L$~~ . The discharge value depends on  
 19 the time constant. The reactance of  
 20  $C$  is very very less than  $R_L$ .

2020 JANUARY

Wk	M	T	W	T	F	S	S
1		1	2	3	4	5	6
2	6	7	8	9	10	11	12
3	13	14	15	16	17	18	19
4	20	21	22	23	24	25	26
5	27	28	29	30	31		