

SEM. IV, paper- CC10

Two terminal devices and their applications
(Specially: **Efficiency of Rectifier**)

Mr. Soumya Das
Dept. physics, Bhatler College

Lecture-III

★ Efficiency of Fullwave Rectifier:—

As $P_{dc} = I_{dc}^2 R_L$ [When R_L is the load resistance of full wave rectifier circuit]

For full wave rectifier,

$$I_{dc} = \frac{2I_0}{\pi} \quad \text{--- (ii)}$$

Using (i) in (ii) we get

$$P_{dc} = \left(\frac{2I_0}{\pi}\right)^2 R_L$$

$$\Rightarrow P_{dc} = \frac{4I_0^2}{\pi^2} R_L \quad \text{--- (iii)}$$

Now $P_{ac} = I_{rms}^2 (R_L + r_d)$ [$r_d \Rightarrow$ Diode resistance]

As $R_L \gg r_d$ so $R_L + r_d \approx R_L$

$$\Rightarrow P_{ac} = I_{rms}^2 R_L \quad \text{--- (iv)}$$

For full wave rectifier,

$$I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{--- (v)}$$

Using (v) in (iv)

$$P_{ac} = \left(\frac{I_0}{\sqrt{2}}\right)^2 R_L$$

$$\Rightarrow P_{ac} = \frac{I_0^2}{2} R_L \quad \text{--- (vi)}$$

$$98 \text{ Now } P_{ac} = I_{rms}^2 (R_L + r_d)$$

99 where r_d is diode resistance.

100 When $R_L \gg r_d$, then $R_L + r_d \approx R_L$

$$101 \text{ So, } P_{ac} = I_{rms}^2 R_L \quad \text{--- (iv)}$$

$$102 \text{ Now } I_{rms} = \frac{I_0}{2} \quad \text{--- (v)}$$

103 Using (v) in (iv)

$$104 P_{ac} = \left(\frac{I_0}{2}\right)^2 R_L$$

$$105 \Rightarrow P_{ac} = \frac{I_0^2}{4} R_L \quad \text{--- (vi)}$$

$$106 \text{ As } \eta = \frac{P_{dc}}{P_{ac}} \quad \text{--- (vii)}$$

107 Using (vi) and (vii) in (vii), we get

$$108 \eta = \frac{\frac{I_0^2 R_L}{\pi^2}}{\frac{I_0^2 R_L}{4}}$$

$$\Rightarrow \eta = \frac{4}{\pi^2} = 0.406 = 40.6\%$$

Efficiency of Rectifier and Efficiency of half wave and Full wave rectifier.

Efficiency of rectifier is defined as the ratio of DC power to the applied input AC power.

$$\text{Rectifier Efficiency} = \frac{\text{DC output power}}{\text{AC input power}}$$

$$\Rightarrow \eta = \frac{P_{dc}}{P_{ac}}$$

* Efficiency of Half wave rectifier:—

In half wave rectifier,

$$P_{dc} = I_{dc}^2 R_L \quad \text{--- (i)}$$

[where R_L is load resistance of half wave rectifier circuit]

But $I_{dc} = \frac{I_0}{\pi}$ where I_0 is peak value of AC

using (ii) in (i)


$$P_{dc} = \left(\frac{I_0}{\pi}\right)^2 R_L$$

$$\Rightarrow P_{dc} = \frac{I_0^2}{\pi^2} R_L \quad \text{--- (iii)}$$

$$\text{As } \eta = \frac{P_{dc}}{P_{ac}} = \frac{\frac{4I_0^2 R_L}{\pi^2}}{\frac{I_0^2}{2} R_L} = \frac{8}{\pi^2}$$

$$\therefore \eta = 0.812 = 81.2\%$$

Capacitor Filter (C-filter)

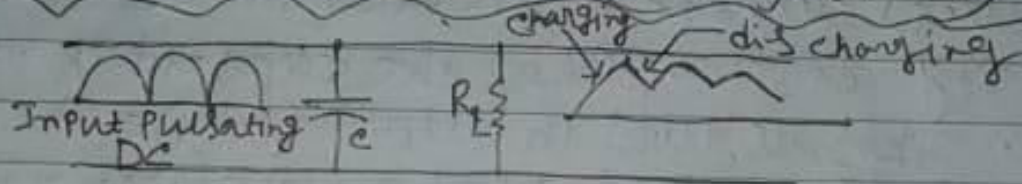

A capacitor-input filter is a filter ckt in which the first element is capacitor connected in parallel with the output of the rectifier in a linear power supply. The capacitor increases the dc voltage and decreases the ripple voltage components of the output. The capacitor is often referred to as a smoothing capacitor. This capacitor is often followed by other alternating series and parallel alternating filter elements to further reduce ripple voltage, or adjust dc voltage. It may also be followed by a voltage regulation regulator which virtually eliminates any remaining ripple voltage and adjusts the dc voltage output very precisely to match the dc voltage required by the ckt.

Operation: - During the time the rectifier is conducting

and the potential is higher than the charge across the capacitor, the capacitor will store energy from the transformer, when the output of the rectifier falls

below the charge on the capacitor, the capacitor will discharge energy into the ckt. Since the rectifier

conducts current only in the forward direction, any energy discharged by the capacitor will flow into the load. This results in output of a DC voltage upon

which is superimposed a waveform referred to as a sawtooth wave is a convenient linear approximation

to the actual waveform which is exponential for both charge and discharge. The crests

of the sawtooth wave will be more rounded when the dc resistance of the transformer

secondary is higher. The time constant $R_C C$ will be large. ~~The reactance is very very less than~~

~~than R_L~~ . The discharge value depends on the time constant. The reactance of

C is very very less than R_L .