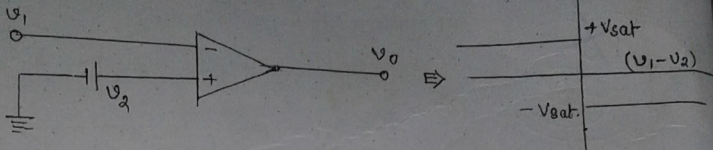


The solution of above differential equation can now be obtained at the output of T_2 with the keys K_1 and K_2 opened and K_3 closed simultaneously by means of a relay at $t=0$.

(11)* Comparator:



The comparator is a circuit which can compare two voltages.

Explanation: As long as $v_1 < v_2$ the output voltage v_0 goes to maximum positive saturation voltage ($+V_{sat}$).


As v_1 crosses v_2 towards the region $v_1 > v_2$, the op-amp output switches to the negative saturation value ($-V_{sat}$).

Thus by looking at the output voltage, we can instantly identify whether $v_1 > v_2$ or $v_1 < v_2$.

18 Schmitt trigger: < Regenerative comparator >

A comparator which uses positive or regenerative feedback and exhibits the phenomena of hysteresis is called a regenerative comparator; more commonly a Schmitt trigger.

Circuit —

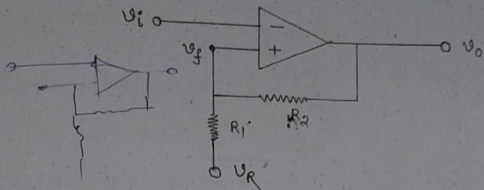

A schmitt trigger circuit using an op amp is shown in figure.

The input voltage v_i is applied to the inverting terminal and the feedback voltage is applied to the non-inverting terminal.

i) When $v_i < v_f$, the output v_o is at positive saturation level ($+V_{sat}$)

Then using superposition principle we get -

$$v_f = \frac{R_2}{R_1 + R_2} v_R + \frac{R_1}{R_1 + R_2} \cdot V_{sat} = v_1 \text{ (say)}$$

If now v_i is now increased then output remains constant at V_{sat} and $v_f = v_1$ (constant) until $v_i = v_1$. At this critical (threshold) or triggering voltage, the output regeneratively switches to " $-V_{sat}$ ".

ii) When $v_i > v_f$, the output v_o is at negative saturation level ($-V_{sat}$).

Using superposition principle, we get,

$$v_f = \frac{R_2}{R_1 + R_2} v_R - \frac{R_1}{R_1 + R_2} \cdot V_{sat} = v_2 \text{ (say)}$$

If now v_i is decreased the output remains at " $-V_{sat}$ " until and $v_f = v_2$ until $v_i = v_2$. At this triggering voltage, the output regeneratively switches to " $+V_{sat}$ ".

Problems

9

Problem - (1): Suppose a sinusoidal signal $v_i = 10 \sin 2000\pi t$ mV is applied to the input of OPAMP ^{Integrator} inverter with $R = 10 \text{ M}\Omega$ and $C = 10 \text{ nF}$. Find the output voltage.


Solution: Output of OPAMP ^{Integrator} inverter $v_o = -\frac{1}{RC} \int_0^t v_i dt$

$$\begin{aligned} \therefore v_o &= -\frac{1}{10 \text{ M}\Omega \times 10 \text{ nF}} \int_0^t 10 \sin 2000\pi t \cdot dt \text{ mV} \\ &= -\frac{0.10}{100000\pi} [-\cos 2000\pi t]_0^t \\ &= \frac{1}{2000\pi} [\sin 2000\pi t - 1] \text{ mV} \end{aligned}$$

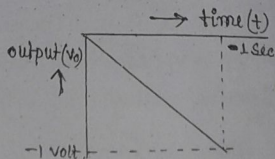Problem - (2): If the input to the OP-AMP integrator is a d.c. of 1, find the nature of output voltage. Assume $R = 1 \text{ M}\Omega$ and


Solution: Output of OP-AMP integrator,

$$\begin{aligned} v_o &= -\frac{1}{RC} \int_0^t v_i dt \\ &= -\frac{1}{10^6 \times 10^{-6}} \int_0^t 1 \cdot dt \\ &= -t \text{ volt} \end{aligned}$$



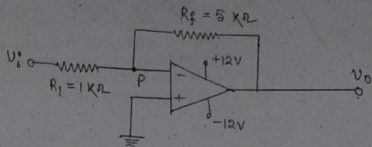Problem - (3):
V.U. - 2006

For the inverting OP-AMP circuit given below, find out the output voltage, input resistance and input current, if the input voltage is 1.5 V. d.c.




$$\text{Output voltage } v_o = - \frac{R_f}{R_1} v_i = - \frac{5}{1} \times 1.5 \text{ volt} = -7.5 \text{ volt.}$$

$$\text{Input resistance } R_i = R_1 = 1 \text{ k}\Omega$$

$$\text{Input current } i = \frac{v_i - v_p}{R_1} = \frac{(1.5 - 0) \text{ volt}}{1 \text{ k}\Omega} = 1.5 \text{ mA.}$$

Problem - (4): For the circuit shown in figure, calculate the output voltage
V.U. - 2009

(b)

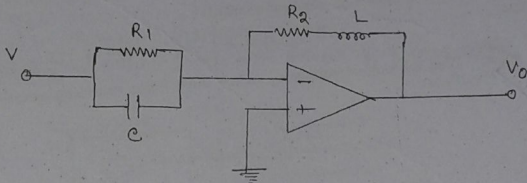

$$Z_1 = R_1 \parallel \frac{1}{j\omega C} = \frac{R_1 + j\omega C}{j\omega C} = \frac{j\omega R_1 - \omega C}{R_1 \omega C}$$

$$Z_f = R_2 + j\omega L$$

$$\begin{aligned} \text{Output of inverting amplifier, } v_o &= - \frac{Z_f}{Z_1} v \\ &= \frac{R_2 + j\omega L}{R_1 + j\omega C} \times j\omega R_1 \omega C \times v \\ &= j \left(\frac{R_2 + j\omega L}{R_1 + j\omega C} \right) R_1 \omega C \cdot \text{volt} \end{aligned}$$

$$\frac{R_1 + \frac{1}{j\omega C}}{R_1 + j\omega C}$$

$$\frac{R_1 + j\omega L}{R_1 + j\omega C} \times j\omega R_1 \omega C$$

2. The noninverting amplifier circuit of Fig. 14.7 has $R_f = 5 \text{ k}\Omega$ and $R_1 = 2 \text{ k}\Omega$. What is the voltage gain?

Ans. The voltage gain is

$$A_v = 1 + \frac{R_f}{R_1} = 1 + \frac{5}{2} = 3.5$$

3. When a voltage $v_1 = +40 \mu\text{V}$ is applied to the noninverting input terminal and a voltage $v_2 = -40 \mu\text{V}$ is applied to the inverting input terminal of an OP AMP, an output voltage $v_0 = 100 \text{ mV}$ is obtained. But, when $v_1 = v_2 = +40 \mu\text{V}$, one obtains $v_0 = 0.4 \text{ mV}$. Calculate the voltage gains for the difference and the common-mode signals, and the common-mode rejection ratio.

Ans. In the first case, the difference signal is $v_d = v_1 - v_2 = 40 - (-40) = 80 \mu\text{V}$ and the common-mode signal is $v_c = (v_1 + v_2)/2 = (40 - 40)/2 = 0$. The output voltage is

$$v_0 = A_d v_d + A_c v_c \quad (i)$$

Where A_d and A_c are the voltage gains for the difference signal and the common-mode signal, respectively. Substituting the values of v_0 , v_d and v_c for the first case in (i), we obtain

$$100 \times 10^3 = A_d \times 80 + A_c \times 0.$$

or,
$$A_d = \frac{10^5}{80} = 1250$$

In the second case, $v_d = v_1 - v_2 = 40 - 40 = 0$ and $v_c = (v_1 + v_2)/2 = (40 + 40)/2 = 40 \mu\text{V}$. Putting the values in (i) gives

$$0.4 \times 10^3 = A_d \times 0 + A_c \times 40$$

or,
$$A_c = \frac{0.4 \times 10^3}{40} = 10$$

The common-mode rejection ratio is

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right| = \frac{1250}{10} = 125.$$

4. Find the output voltage v_0 of the three-input summing amplifier circuit of Fig. 14.22.

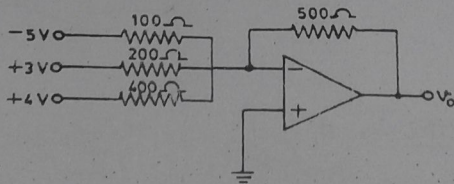


Fig 14.22

Handwritten notes in blue ink at the bottom left corner of the page.

Ans. Equation (14.17) gives for the output voltage

$$v_o = - \left(\frac{500}{100} \times -5 + \frac{500}{200} \times 3 + \frac{500}{400} \times 4 \right) \\ = - (-25 + 7.5 + 5) = 12.5 \text{ V}$$

5. Compute the voltage gain for the amplifier shown in Fig. 14.23. Find the output voltage v_{out} if the input voltage is $v_{in} = 0.5 \sin 100 \pi t$ volt. (C.U. 1996).

Ans. The voltage gain of the given inverting amplifier is

$$A = - \frac{50 \text{ k}\Omega}{1 \text{ k}\Omega} = -50.$$

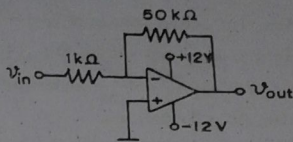


Fig. 14.23

If the operation were entirely linear, the output voltage would have been

$$v_{out} = A v_{in} = -50 \times 0.5 \sin 100 \pi t = -25 \sin 100 \pi t \text{ V.}$$

But since the supply voltage is $\pm 12\text{V}$, the OP AMP is saturated when $|v_{out}|$ attains 12 V . Let at time $t = t_0$, $v_{out} = -12\text{V}$. Then

$$-12 = -25 \sin 100 \pi t_0$$

$$\text{or, } t_0 = \frac{1}{100 \pi} \sin^{-1} \left(\frac{12}{25} \right) = 1.59 \times 10^{-3} \text{ s.}$$

Thus over the entire cycle, we have

$$v_{out} = -25 \sin 100 \pi t \text{ V when } 0 \leq t \leq t_0 \\ = -12 \text{ V when } t_0 \leq t \leq (0.01 - t_0) \\ = -25 \sin 100 \pi t \text{ V when } 0.01 - t_0 \leq t \leq 0.01 + t_0 \\ = +12 \text{ V when } 0.01 + t_0 \leq t \leq 0.02 - t_0 \\ = -25 \sin 100 \pi t \text{ V when } 0.02 - t_0 \leq t \leq 0.02 \text{ s.}$$

The variation of v_{out} with t over a full cycle ($0 \leq t \leq 0.02\text{s}$) is shown in Fig. 14.24.

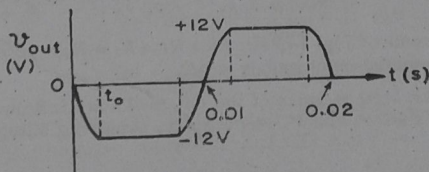


Fig. 14.24

6. A ramp voltage of 1.5 V (as shown in Fig. 14.25) per millisecond is applied to an OP AMP differentiator having $R = 2 \text{ k}\Omega$ and $C = 0.01 \text{ }\mu\text{F}$. Find the output voltage and its waveform. (C.U. 1999)

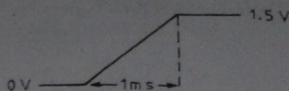


Fig. 14.25

Ans. The output voltage is $v_0 = -RC \frac{dv_i}{dt}$

Here v_i is as shown in Fig. 14.25. For

$$0 < t < 1 \text{ ms}, \frac{dv_i}{dt} = \frac{1.5 \text{ V}}{1 \text{ ms}}, \text{ otherwise } \frac{dv_i}{dt} = 0.$$

$$\text{Also, } RC = 2 \times 0.01 \text{ ms.}$$

$$\text{Hence } v_0 = -0.02 \times 1.5 = -0.03 \text{ V} \\ = -30 \text{ mV for } 0 < t < 1 \text{ ms. Otherwise, } v_0 = 0.$$

The waveform of v_0 is shown in Fig. 14.26.

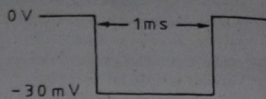


Fig. 14.26

7. In the circuit of Fig. 14.26A, express v_0 in terms of v_1 and v_2 .

Ans. All the voltages are measured with respect to ground. The voltage at the point b is

$$v = \frac{R_2}{R_1 + R_2} v_2.$$

The voltage at the point a is also v owing to the infinite voltage gain of the OP AMP. The current through R_3 is

$i = (v_1 - v)/R_3$. This current charges the capacitance C , and so the capacitor voltage is

$$v - v_0 = \frac{1}{C} \int_0^t i dt$$

$$\text{or, } \frac{R_2 v_2}{R_1 + R_2} - v_0 = \frac{1}{CR_3} \int_0^t \left(v_1 - \frac{R_2 v_2}{R_1 + R_2} \right) dt$$

$$\text{or, } v_0 = \frac{R_2 v_2}{R_1 + R_2} - \frac{1}{CR_3} \int_0^t \left(v_1 - \frac{R_2 v_2}{R_1 + R_2} \right) dt.$$

8. For the circuit of Fig. 14.26B, $R_1 = R_3 = R_4 = R_5 = 10 \text{ k}\Omega$, and $R_2 = 100 \text{ }\Omega$. Find the differential mode gain $A = v_0/(v_1 - v_2)$.

Ans. Since the voltage gains of the OP AMPs are infinite, the voltages of the points X and Y are V_1 and V_2 , respectively. Applying Kirchoff's current law at X , we obtain

$$\frac{V_1}{R_1} + \frac{V_1 - V}{R_3} + \frac{V_1 - V_2}{R_2} = 0$$

✓ **Problem 4.** If the circuit of Fig. 10.10-1 has $R_1 = 10 \text{ k}\Omega$ and $R_2 = 50 \text{ k}\Omega$ what would be the output voltage for an input (a) $v_s = 1 \text{ V}$ and (b) $v_s = 3 \text{ V}$. Assume OP AMP supply voltages to be $\pm 12 \text{ V}$

Solution:

(a) The output voltage

$$v_0 = \left(1 + \frac{R_2}{R_1}\right) v_s = \left(1 + \frac{50}{10}\right) \cdot 1 \text{ V} \\ = 6 \text{ V}$$

(b) If we put $v_s = 3 \text{ V}$ in the above relation v_0 comes out to be 18 V . But actually the OP AMP, in this case, saturates and v_0 becomes very nearly equal to $+12 \text{ V}$ (supply voltage).

✓ **Problem 5.** Calculate the output voltage of the OP AMP summing amplifier of Fig. 10.10-3 with three inputs $v_1 = 1 \text{ V}$, $v_2 = -2 \text{ V}$ and $v_3 = +3 \text{ V}$. Assume $R_1 = R_2 = R_3 = 500 \text{ k}\Omega$ and $R_f = 1 \text{ M}\Omega$.

Solution:

$$v_0 = -\frac{R_f}{R_1}(v_1 + v_2 + v_3) \\ = -\frac{1 \text{ M}\Omega}{500 \text{ k}\Omega}(1 - 2 + 3) \text{ V} \\ = -2 \times 2 \text{ V} \\ = -4 \text{ V}$$

✓ **Problem 6.** Suppose a sinusoidal signal $v_s = 10 \sin 2000\pi t \text{ mV}$ is applied to the input of the OP AMP integrator of Fig. 10.10-5 with $R = 1 \text{ M}\Omega$ and $C = 1 \mu\text{F}$. Find the output voltage.

Solution:

$$v_0 = -\frac{1}{CR} \int_0^t v_s dt = \frac{1}{(1 \mu\text{F})(1 \text{ M}\Omega)} \int_0^t 10 \sin 2000\pi t dt \text{ mV} \\ = -0.10 \left[\frac{-\cos 2000\pi t}{2000\pi} \right]_0^t \text{ mV} \\ = \frac{1}{200\pi} [\cos 2000\pi t - 1] \text{ mV}$$

✓ **Problem 7.** If the input to the OP AMP integrator of Fig. 10.10-5 is a d.c. of 1 V , find the nature of output voltage. Assume $R = 1 \text{ M}\Omega$ and $C = 1 \mu\text{F}$.

Solution:

$$v_0 = -\frac{1}{CR} \int_0^t v_s dt = -\frac{1}{1 \mu\text{F}} \cdot 1 \text{ M}\Omega \int_0^t 1 \cdot dt \text{ volt} \\ = -t \text{ volt}$$

Thus the output is a linearly decreasing ramp voltage. The output ramp reaches -1 V in 1 second (Fig. 10.P-7).

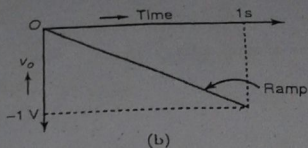
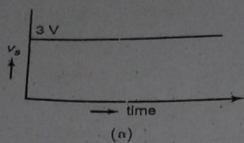


Fig. 10.P-7: Integrator (a) Input (b) Output

Problem 8. A ramp voltage of 1.5 V per millisecond (as shown in Fig. 10.P-8(a)) is applied to an OP AMP differentiator with $F = 2\text{ k}\Omega$ and $C = 0.01\text{ }\mu\text{F}$. Find the output voltage and its waveform. (C.U. 1999)

Solution: From Fig. 10.P-8(a)

$$\frac{dv_s}{dt} = 1.5\text{ V/ms within the } 1\text{ ms range}$$

$$= 0\text{ outside the } 1\text{ ms range}$$

Now output

$$v_o = -CR \frac{dv_s}{dt}$$

$$= -(0.01\text{ }\mu\text{F})(2\text{ k}\Omega) \times 1.5\text{ V/ms.}$$

$$= -0.0 \times 10^{-6} \times 2 \times 10^3 \times 1.5 \times 10^3\text{ V}$$

$$= -0.03\text{ V}$$

$$= -30\text{ mV within the } 1\text{ ms range}$$

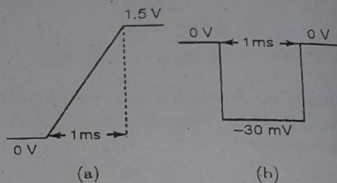


Fig. 10.P-8: Integrator (a) Input (b) Output

$v_o = 0$ outside the 1 ms range

Therefore, the output waveform will be as shown in Fig. 10.P-8(b).

Problem 9. What is the output voltage in the circuit of Fig. 10.P-9? Explain the operation of circuit. (C.U. 2000)

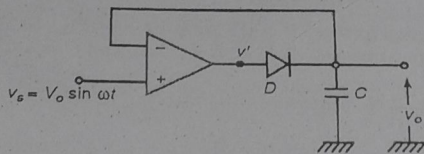


Fig. 10.P-9

Solution: If $v_s > v_0$ the OP AMP output v' is positive. The diode D then conducts and capacitor C is charged to the value of the input because the gain of the circuit is unity. In this way the capacitor is charged to the peak value (V_0) of the input. When v_s goes below the capacitor voltage OP AMP output v' becomes negative. The diode then becomes reverse-biased and stops conducting. However the capacitor voltage remains at the peak value (V_0) of the input. Thus the circuit acts as a peak detector.

✓ Problem 10. If a sinusoidal voltage $v_s = 10 \sin 2000\pi t$ mV is applied to the input of the OP AMP differentiator of Fig. 10.10-6 with $C = 1 \mu\text{F}$ and $R = 100 \text{ k}\Omega$, what would be the output voltage?

$$\begin{aligned} \text{Solution: } v_0 &= -CR \frac{dv_s}{dt} = -10^{-6} \times 10^5 \times \frac{d}{dt} (10 \sin 2000\pi t) \text{ mV} \\ &= -2000\pi \cos 2000\pi t \text{ mV} \\ &= -2\pi \cos 2000\pi t \text{ V} \end{aligned}$$

✓ Problem 11. Consider the OP AMP amplifier of Fig. 10.9-1 with $R_1 = 1 \text{ k}\Omega$, $R_2 = 50 \text{ k}\Omega$ and OP AMP supply voltages $\pm 12 \text{ V}$. Compute the gain and find the output if input is $V_s = 0.5 \sin 100\pi t$ volt. (C.U. 1996)

Solution: Gain of the amplifier is

$$-\frac{R_2}{R_1} = -50$$

If the OP AMP were within linear region over the whole range of input, then the output would have been

$$v_0 = -50v_s = -25 \sin 100\pi t \text{ volt}$$

Since the supply voltages are $\pm 12 \text{ V}$, the output saturates at $\pm 12 \text{ V}$. So the output will be sinusoidal voltage $-25 \sin 100\pi t$ volt with sharp clippings at $\pm 12 \text{ V}$ as shown in Fig. 10.P-11.

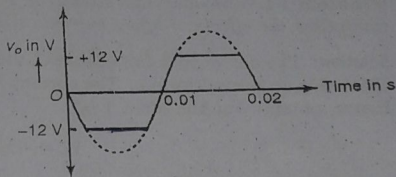


Fig. 10.P-11

✓ Problem 12. Draw a circuit using one or more OP AMP whose output v_0 is given as $v_0 = 4v_1 + 6v_2$, where v_1 and v_2 are two input signals. (B.U. 1999)

$$\text{Solution: In Fig. 10.P-12 } v' = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2\right) = -(4v_1 + 6v_2)$$

$$\text{Now the inverter output } v_0 = -v' = 4v_1 + 6v_2$$

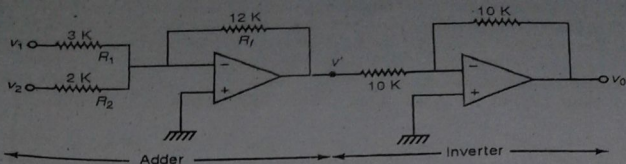


Fig. 10.P-12

Problem 13. What does the circuit of Fig. 10.P-13 do? Explain.

Solution: The input v_1 drives an inverter of gain unity. So the output of first stage is $-v_1$. The second stage is summing amplifier with gain unity for each input. Thus $v_0 = v_1 - v_2$ and the circuit acts as a subtractor.

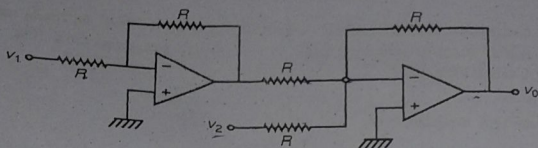


Fig. 10.P-13

Problem 14. Consider the circuit of Fig. 10.P-14. Find the value of R_3 which minimises the effects of offset current. Assume output impedance to be zero.

Solution: The d.c. output impedance of the OP AMP is low and the output terminal is effectively at ground for d.c. The current I_1 passes the resistors R_1 and R_2 in parallel. Hence, potential at the point 1 is

$$V_1 = -I_1 \cdot \frac{R_1 R_2}{R_1 + R_2}$$

The potential at the point 2 is

$$V_2 = -I_2 \cdot R_3$$

∴ The output voltage of the amplifier is given by

$$\begin{aligned} V_0 &= A(V_2 - V_1) \\ &= A \left(I_2 \frac{R_1 R_2}{R_1 + R_2} - I_2 R_3 \right) \end{aligned}$$

Thus $V_0 = 0$ if we choose $I_1 \cdot \frac{R_1 R_2}{R_1 + R_2} = I_2 R_3$

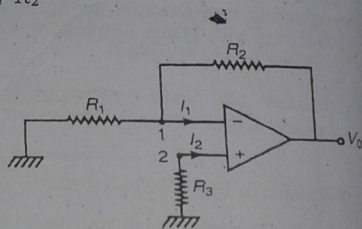


Fig. 10.P-14

18

Therefore $R_3 = \frac{R_1 R_2}{R_1 + R_2}$ is the desired value of R_3 if $I_1 \approx I_2$. Note that R_3 has no effect on the virtual ground approximation because no a.c. signal current flows through it.

- ✓ **Problem 15.** Consider the differential-input amplifier of Fig. 10.P-15. Assuming infinite input resistance, zero output resistance and finite differential gain $A_v = V_0/(V_1 - V_2)$ show that closed loop gain is given by $A_{vf} = \frac{A_v}{1 + \frac{A_v}{n+1}}$. Discuss the case $A_v \rightarrow \infty$.

Solution: $V_2 = \frac{V_0 \cdot R}{nR + R} = \frac{V_0}{n+1}$

$$V_1 = V_s$$

$$V_0 = A_v(V_1 - V_2)$$

$$= A_v \left(V_s - \frac{V_0}{n+1} \right)$$

$$\text{or } A_{vf} = \frac{V_0}{V_s} = \frac{A_v}{1 + \frac{A_v}{n+1}}$$

In the limit $A_v \rightarrow \infty$, $A_{vf} \rightarrow n+1$.

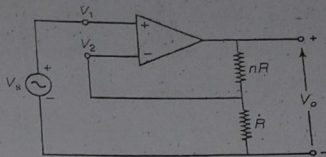


Fig. 10.P-15

- ✓ **Problem 16.** In a differential amplifier with two inputs, the output is 2.01 mV when the inputs are $110 \mu\text{V}$ and $90 \mu\text{V}$ but the output is 2 mV when inputs are $10 \mu\text{V}$ and $-10 \mu\text{V}$. Find the CMRR of the amplifier. (B.U. 1999)

Solution: In the second case $v_d = 20 \mu\text{V}$ and $v_c = 0$

$$v_0 = A_d v_d + A_c v_c \quad \text{or} \quad 2 \text{ mV} = A_d \times 20 \mu\text{V}$$

$$\therefore A_d = 100$$

In the first case,

$$v_d = 20 \mu\text{V}; \quad v_c = \frac{v_1 + v_2}{2} = 100 \mu\text{V}$$

$$\therefore v_0 = A_d v_d + A_c v_c$$

$$\text{or, } 2.01 \text{ mV} = 100 \times 20 \mu\text{V} + A_c \times 100 \mu\text{V}$$

$$\text{or, } A_c = \frac{1}{10}$$

$$\therefore \text{CMRR} = \left| \frac{A_d}{A_c} \right| = 1000$$

✓ **Problem 17.** Show that the output voltage of the circuit in Fig. 10.P-17 is given by

$$v_0 = v_2 \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} - v_1 \cdot \frac{R_2}{R_1}$$

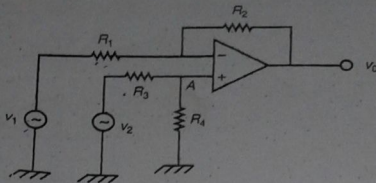


Fig. 10.P-17

(cf. B.U. 2004)

Solution: We can find v_0 by using superposition principle. The output voltage due to v_1 alone is

$$v_{01} = -\frac{R_2}{R_1} \cdot v_1$$

Voltage at the non-inverting terminal is $v_A = \frac{v_2 \cdot R_4}{R_3 + R_4}$. Therefore, the output voltage due to v_2 alone is

$$v_{02} = \left(1 + \frac{R_2}{R_1}\right) v_A = v_2 \cdot \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1}$$

Hence by the superposition principle, the resultant output voltage is

$$v_0 = v_{01} + v_{02} = v_2 \cdot \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} - v_1 \cdot \frac{R_2}{R_1}$$

✓ **Problem 18.** Find the output voltage v_0 in the circuit of Fig. 10.P-18. (GATE 2001)

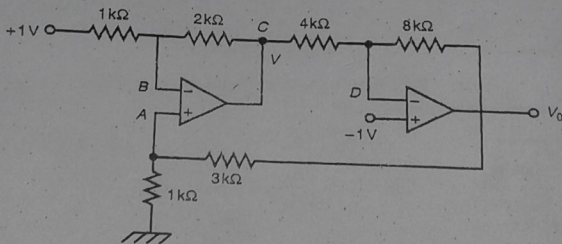



Fig. 10.P-18

[Fun.Prin.Elec. 25]

Wien-Bridge Oscillator

V.U - 2001, 2003, 2007

Oscillators using tuned (LC) circuits are not suitable for generating low frequency (LF) signals because then the physical dimensions of L and C would be large and hence the device would be costly. That is why for generating low frequency signals RC oscillators are used. Wien-Bridge oscillator is one such RC oscillator which is widely used in the laboratory as an audio frequency (AF) signal generator.

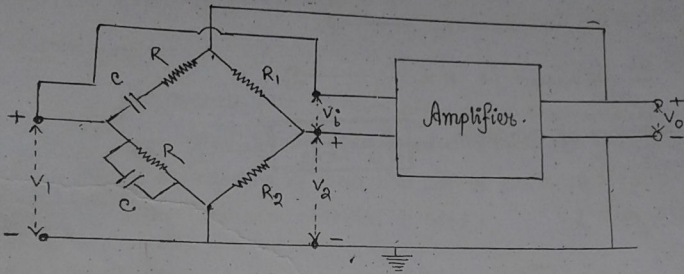

The circuit diagram of a Wien-Bridge oscillator using amplifier is shown in figure. Either OPAMP or BJT or FET can be used as amplifier.

The frequency determining circuit of the amplifier is a Wien-bridge circuit. The R-C combination and the resistors R_1 and R_2 form the four ~~arm~~ arms of a Wien-bridge.

The ^{Input} output V_i of the bridge is amplified by the amplifier. The output V_0 of the amplifier becomes the bridge supply voltage.

When the bridge is exactly balanced, $V_i = 0$. But for sustained oscillation, V_i must be nonvanishing. This is done by adjusting the ratio between the resistances R_1 and R_2 .

Frequency of oscillation:

When the bridge is balanced, we have

$$\frac{R_1}{R_2} = \frac{Z_1}{Z_2} = \frac{R + \frac{1}{j\omega C}}{R \parallel \frac{1}{j\omega C}} = \frac{R + \frac{1}{j\omega C}}{\frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{(R + \frac{1}{j\omega C})^2}{R \cdot \frac{1}{j\omega C}}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{R^2 - \frac{1}{\omega^2 C^2} + \frac{2R}{j\omega C}}{R \cdot \frac{1}{j\omega C}}$$

$$\Rightarrow \frac{R_1}{R_2} = 2 + j \frac{R^2 - \frac{1}{\omega^2 C^2}}{R \cdot \omega C} \quad \text{--- (1)}$$

Equating the real and imaginary part of above equation,

$$\frac{R_1}{R_2} = 2 \quad \text{i.e.} \quad R_1 = 2R_2 \quad \text{--- (2)}$$

and $\frac{R^2 - \frac{1}{\omega^2 C^2}}{R \cdot \omega C} = 0$ i.e. $R = \frac{1}{\omega C}$ --- (3)

The frequency of oscillation,

$$f = \frac{1}{2\pi RC} \quad \text{--- (4)}$$

Amplifier gain:

When the bridge is balanced, the voltage across the two lower arms of the bridge must be equal i.e.

$$V_1 = V_2 = \frac{R_2}{R_1 + R_2} V_0 \quad \text{--- (5) as } V_2 = \frac{R_2}{R_1 + R_2} V_0 \quad \therefore A = \frac{V_0}{V_1} = \frac{R_1 + R_2}{R_2}$$

Again, at balance condition, $\frac{R_1}{R_1 + R_2} = \frac{1}{3}$ using equation (2)

$$\therefore \frac{V_1}{V_0} = \frac{V_2}{V_0} = \frac{1}{3} \quad \text{--- (6)}$$

oscillation to occur, $V_i \neq 0$ then the ratio $\frac{R_2}{R_1 + R_2}$ must be less.

Let $\frac{R_2}{R_1 + R_2} = \frac{1}{3} - \frac{\delta}{8}$ Where δ is a number greater than 3.

$$\therefore \frac{V_0}{V_0} = \frac{1}{3} - \frac{\delta}{8} \quad \text{--- (7)}$$

had also

(22)

As the bridge is unbalanced by adjusting R_1/R_2 ,
the ratio $\frac{V_1}{V_0}$ remains $\frac{1}{3}$.

but the ratio $\frac{V_2}{V_0}$ becomes, $\frac{V_2}{V_0} = \frac{1}{3} - \frac{1}{6}$

Thus feedback voltage is, $V_f = V_1 - V_2 = (\frac{1}{3} - \frac{1}{3} + \frac{1}{6}) V_0 = \frac{V_0}{6}$

Clearly, V_i and V_0 are in phase and feedback fraction $\beta = \frac{V_f}{V_0} = \frac{1}{6}$

Thus the condition $\beta A = 1$ is satisfied by making the gain of the amplifier $A = 6$ where δ is greater than 3.

Thus the amplifier used in Wien bridge oscillator must have a gain greater than 3.

Advantages:

- i) The overall gain is high since a two stage amplifier is used.
- ii) The circuit gives a very good sine wave output.
- iii) The frequency of oscillation can be easily varied.
- iv) The frequency stability is good.

Disadvantages:

- i) The circuit is not capable of generating very high frequency.
- ii) The number of components required for a two stage amplifier is very large.

Problem:

V.U - 2005

A Wien-bridge oscillator has a frequency of 1000 Hz and a capacitance of 100 pF. Find the resistance:

if the amplifier gain is 10, find the ratio of resistances in the other arms.

Solution: $f = \frac{1}{2\pi RC} \Rightarrow R = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 1000 \times 10^{-10}} \text{ ohm}$
 $= 1.59 \text{ M}\Omega$

Gain of the amplifier $A = \frac{R_1 + R_2}{R_2} \Rightarrow 10 = \frac{R_1}{R_2} + 1 \Rightarrow \boxed{\frac{R_1}{R_2} = 9:1}$