

SEM. IV, paper- CC10

OPAMP

Mr. Soumya Das
Dept. physics, Bhatler College

Lecture-V

20/20

January

OPAMP

①

FRIDAY

31

5th Week • 031-335

⁰⁸ OPAMP :- The operational amplifier abbreviated as "OPAMP", is a direct coupled high gain, differential input ⁰⁹ amplifier. The significance of the term "operational" is that ¹⁰ can perform mathematical operations such as - Summation, Sub-traction, differentiation and integration.

¹¹ It is also used in signal amplification, impedance transformation, oscillators, voltage regulator, analog to digital ¹² converter and digital to analog converter etc.

⊗ Characteristics of an ideal "OPAMP" :-

An ideal OPAMP has following characteristics.


- ⁰³ i) Infinite input impedance.
- ⁰⁴ ii) Zero output impedance.
- ⁰⁵ iii) Infinite voltage gain.
- ⁰⁶ iv) Infinite band width.
- v) Characteristics not drifting with temp. r.
- vi) Perfect balance [i.e. when equal voltages are applied to the input terminals then out voltage is zero.]

08 Characteristics of a practical OPAMP:

- 09 i) Finite but large input impedance.
- 10 ii) Non-zero but small output impedance.
- 11 iii) Finite but large voltage gain.
- 12 iv) Finite but large bandwidth.
- 01 v) Characteristics drift with temp- T .
- 02 vi) Imperfect balance.

03 Circuit Symbol of OPAMP:

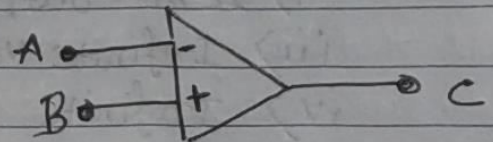04 It has two input terminals A, B and
05 one output terminal C.



06 The terminal "A" is known as inverting terminal, which is labelled
02 Sunday by "-". The negative sign indicates that a signal applied at this
terminal, the output becomes reversed polarity.

The terminal "B" is known as non-inverting terminal, which is
labelled by "+". A signal applied to this terminal appears at the
terminal "C" with the same polarity.


08 The ~~out~~ output voltage at c is proportional to the difference of the two signal voltages applied at the two input terminals simultaneously.

09 If V_1 and V_2 are the input signals applied to the non-inverting and inverting terminals respectively, then output voltage of ideal OPAMP is given by, $V_o \propto (V_1 - V_2)$

$$\Rightarrow V_o = A(V_1 - V_2)$$

12 This proportionality constant A is called open loop gain of the OPAMP.

01 * IC form of OPAMP :-

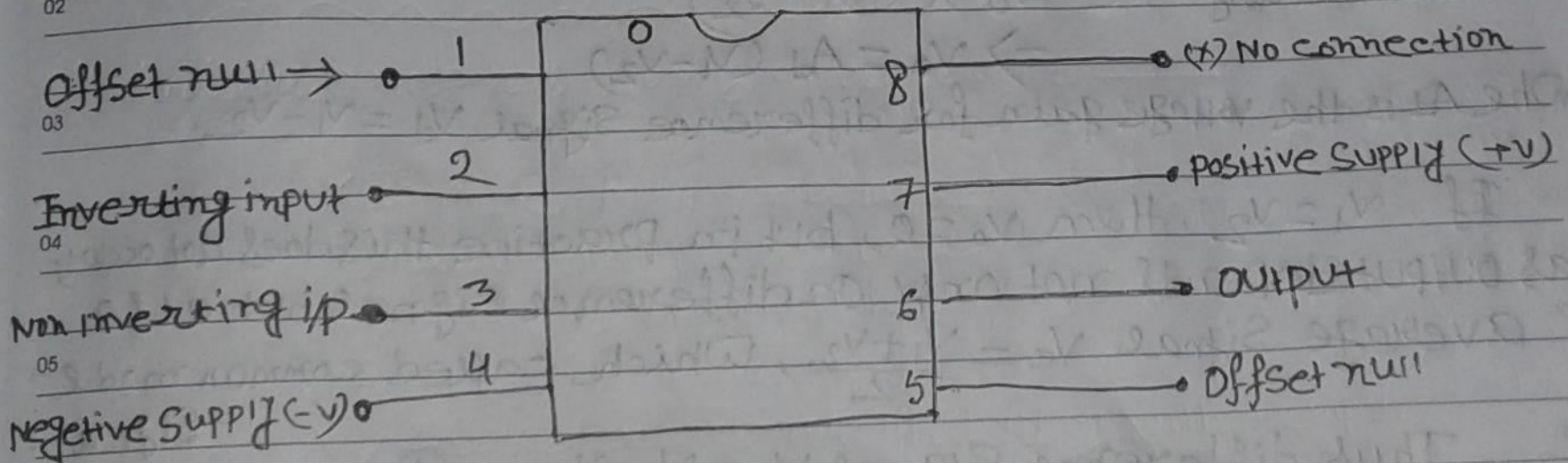

⁰⁸ CMRR is the abbreviation of common mode rejection ratio, which is defined as the ratio of voltage gain for difference signal (A_d) to the voltage gain for common mode signal (A_c)

¹⁰ i.e.
$$CMRR = \left| \frac{A_d}{A_c} \right| = \frac{\text{voltage gain for difference signal}}{\text{voltage gain for common mode signal}}$$

¹¹ Note: - CMRR is often expressed in dB, as

$$CMRR(\text{in dB}) = 20 \log_{10} \left| \frac{A_d}{A_c} \right|$$

¹² Details :- Differential amplifier. — The output voltage of an OPAMP is proportional to the difference of the two signal voltages applied at the two input terminals simultaneously. i.e. $V_o \propto (V_1 - V_2)$

$$\Rightarrow V_o = A_d (V_1 - V_2)$$

Where A_d is the voltage gain for difference signal $V_d = V_1 - V_2$.

⁰⁴ If $V_1 = V_2$, then $V_o = 0$, but in practice this does not occur, as output depends not only on difference signal but also average signal $V_c = \frac{V_1 + V_2}{2}$, which called common mode signal.

⁰⁶ Thus difference signal $V_d = V_1 - V_2$ --- (i)

and common mode signal $V_c = \frac{V_1 + V_2}{2}$ --- (ii)

From equation (i) & (ii), we get $V_1 = V_c + \frac{1}{2} V_d$ --- (iii)

and $V_2 = V_c - \frac{1}{2} V_d$ --- (iv)

If A_1 be the gain when inverting terminal is grounded and A_2 be the gain when non-inverting terminal is grounded